

ECEN 248 - Lab Report

Lab Number: 8

Lab Title: Counters, Clock Dividers, and Debounce Circuits

Section Number: 513

Student's Name: Abhishek Bhattacharyya

Student's UIN: 731002289

Date: 4/12/2023

TA: Hesam Mazaheri

Objectives:

This week's lab project is to gain more experience of sequential circuits by introducing the idea of a binary counter, a major part of a synchronous sequential circuit. This lab explores how to create a binary up-counter using the combinational and sequential components described in previous labs. The lab will also demonstrate the real-world uses of binary counters, such as clock frequency division and I/O debouncing, and it will give you the opportunity to test designs first-hand on the FPGA board.

Design:

All Verilog code used in this lab is included below.

```
1`timescale 1ns/1ps
2`default_nettype none
3
4// This simple module will demonstrate the concept of clock frequency
5// division using a simple counter. We will use behavioral Verilog
6// for our circuit description
7
8module clock_divider(ClkOut, ClkIn);
9
10 // output port needs to be a reg because we will drive it with
11 // a behavioral statement
12 output wire [3:0] ClkOut;
13 input wire ClkIn; // wires can drive regs
14
15 // this is a keyword we have not seen yet
16 // as the name implies, it is a parameter
17 // that can be changed at compile time
18
19 parameter n = 5; // make count 6-bits for now...
20
21 reg [n:0] Count; // count bit width is based on n!
22
23 // simple behavioral construct to describe a counter
24 always@ (posedge ClkIn)
25     Count <= Count + 1;
26
27 // now we need to wire up our ClkOut which is a 4-bit wire
28 // Wire up to most-significant bits
29 assign ClkOut[3:0] = Count[n:n-3];
30
31 initial
32     begin
33         Count <= 0;
34     end
35endmodule
```

Figure 1: Source Code for Clock Divider

```
1`timescale 1 ns/1 ps
2`default_nettype none
3// This is a module for the half adder previously used in Lab 3
4// however this one is using the dataflow aspect of Verilog
5
6module half_adder(S, Cout, A, B);
7    input wire A, B;
8    output wire S, Cout;
9
10    assign Cout = A & B;
11    assign S = A ^ B;
12
13endmodule
```

Figure 2: Source Code for Half Adder

```

1 timescale 1 ns/1 ps
2 default_nettype none
3// This module describes a simple 3-bit up-counter using
4// half-adder modules built in the previous step
5
6module up_counter(Count, Carry2, En, Clk, Rst);
7    // Count output needs to be a reg
8    output reg [2:0] Count;
9    output wire Carry2;
10    // inputs are wires
11    input wire En, Clk, Rst;
12    // intermediate nets
13    wire [2:0] Carry, Sum;
14
15    // here we create and instantiate the wrapper for the 3-bit counter
16    threebit_counter UC1(Sum, Carry2, Count, En);
17    // describe positive edge triggered flip-flops for count
18    // including "posedge Rst" in the sensitivity list
19    // implies an asynchronous reset
20    always@(posedge Clk or posedge Rst)
21        if (Rst) // if Rst == 1'b1
22            Count <= 0; // reset count
23        else // otherwise, latch the sum
24            Count <= Sum;
25
26endmodule
27
28
29
30module threebit_counter(Sum, Carry2, Count, En);
31    // declare the variables
32    input wire En;
33    input wire [2:0] Count;
34    output wire [2:0] Sum;
35    output wire Carry2;
36    wire [2:0] Carry;
37
38    // instantiate and wire up your half-adders here
39    half_adder HA1(Sum[0], Carry[0], En, Count[0]);
40    half_adder HA2(Sum[1], Carry[1], Carry[0], Count[1]);
41    half_adder HA3(Sum[2], Carry[2], Carry[1], Count[2]);
42
43    // wire up carry2 here
44    assign Carry2 = Carry[2];
45endmodule

```

Figure 3: Source Code for Up-Counter and 3-bit Counter

```

1 timescale 1ns / 1ps // specify 1 ns for each delay unit
2 default_nettype none
3
4// this is the top-level module which wires all
5// of our synchronous components together. this module
6// does NOT include synchronizers for the inputs (we
7// will discuss them shortly) so just don't use this in
8// a real application
9
10module top_level(LEDs, SWs, BTNs, FastClk);
11    // all ports will be wires
12    output wire [3:0] LEDs;
13    input wire [1:0] SWs;
14    input wire [1:0] BTNs;
15    input wire FastClk;
16
17    // there are 4 LEDs, 2 switches, and 2 buttons
18    // FastClk is a 1-bit wide input
19
20    // intermediate nets
21    wire [3:0] Clacks;
22    reg SlowClk; // will use an always block for MUX
23
24    // behavioral description of a four-way MUX
25    always@(*) // combinational logic
26        case(SWs) // SWs is a 2-bit bus
27            2'b00: SlowClk = Clacks[0];
28            2'b01: SlowClk = Clacks[1];
29            2'b10: SlowClk = Clacks[2];
30            2'b11: SlowClk = Clacks[3];
31            // use blocking statements for
32            // combinational logic
33        endcase
34
35    // here i instantiated the up counter
36    up_counter UC0(LEDs[2:0], LEDs[3], BTNs[0], SlowClk, BTNs[1]);
37
38    // instantiate the clock divider
39    clock_divider clk_div0(
40        .ClkOut(Clocks),
41        .ClkIn(FastClk)
42    );
43endmodule

```

Figure 4: Source Code for Top-Level

```

1`timescale 1ns / 1ps
2`default_nettype none
3module withDebounce(LEDs, BTN, Clk);
4    output reg [3:0] LEDs;
5    input wire BTN, Clk;
6    /*-this is a keyword we have not seen yet!*/
7    /*-as the name implies, it is a parameter */
8    /* that can be changed at compile time... */
9    parameter n = 5;
10   wire notMsb, Rst, En, Debounced;
11   reg Synchronizer0, Synchronized;
12   reg [n-1:0] Count;
13   reg edge_detect0;
14   wire rising_edge;
15   /*This is just for simulation*/
16   initial
17       LEDs=0;
18   /******
19   /* Debounce circuitry!!! */
20   /******
21   always@(posedge Clk)
22   begin
23       // this sets synchronizer0 to the btn
24       Synchronizer0 <= BTN;
25       // this sets the output of the synchronizer circuit.
26       // synchronized to the synchronizer0 that was set
27       Synchronized <= Synchronizer0;
28   end
29   always@(posedge Clk)
30   // if the reset is on, then the count will be less
31   // than or equal to 0
32   if(Rst)
33       Count <= 0;
34   // if the enable is on, then the count will be less
35   // than or equal to the count plus one
36   else if(En)
37       Count <= Count + 1;
38   // this assigns notMsb with the Count[n-1] being NOT
39   assign notMsb = ~Count[n-1];
40   // this assigns En with the notMsb that was assigned
41   // above and the Synchronized output from the Synchronizer
42   // part of the circuit
43   assign En = notMsb & Synchronized;
44   // this assigns reset with the Synchronized output being NOT
45   assign Rst = ~Synchronized;
46   // this assigned Debounced with the Count[n-1] that was
47   // earlier with the notMsb part of the circuit
48   assign Debounced = Count[n-1];
49   /******
50   /* End of Debounce circuitry!!! */
51   /******
52   always@(posedge Clk)
53   edge_detect0 <= Debounced;
54   assign rising_edge = ~edge_detect0 & Debounced;
55   always@(posedge Clk)
56   if(rising_edge)
57       LEDs <= LEDs + 1;
58 endmodule

```

Figure 5: Source Code for with Debounce

```

1# Switches
2set_property PACKAGE_PIN G15 [get_ports {SWs[0]}]
3set_property IOSTANDARD LVCMOS33 [get_ports {SWs[0]}]
4set_property PACKAGE_PIN P15 [get_ports {SWs[1]}]
5set_property IOSTANDARD LVCMOS33 [get_ports {SWs[1]}]
6
7# Buttons
8# IO_L2B8_T3_34
9set_property PACKAGE_PIN K18 [get_ports {BTN0[0]}]
10set_property IOSTANDARD LVCMOS33 [get_ports {BTN0[0]}]
11set_property PACKAGE_PIN P16 [get_ports {BTN0[1]}]
12set_property IOSTANDARD LVCMOS33 [get_ports {BTN0[1]}]
13
14# LEDs
15# IO_L2B8_T3_35
16set_property PACKAGE_PIN M14 [get_ports {LEDs[0]}]
17set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[0]}]
18set_property PACKAGE_PIN M15 [get_ports {LEDs[1]}]
19set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[1]}]
20set_property PACKAGE_PIN G14 [get_ports {LEDs[2]}]
21set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[2]}]
22set_property PACKAGE_PIN D18 [get_ports {LEDs[3]}]
23set_property IOSTANDARD LVCMOS33 [get_ports {LEDs[3]}]
24
25# Clock signal
26# IO_L11P_T1_SRCC_35
27set_property PACKAGE_PIN K17 [get_ports FastClk]
28set_property IOSTANDARD LVCMOS33 [get_ports FastClk]
29create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports FastClk]

```

Figure 6: Source Code for Top-Level XDC File

Results:

After the first two parts of this experiment were completed, I was able to create and analyze the binary counter. By analyzing the oscilloscope output (shown below), the clock period of each counter within the clock divider module was calculated. These results showed that the counter module was working as expected, dividing the clock signal.

 


Figure 7: Oscilloscope Output

 


Figure 8: Oscilloscope Output with Bus

Conclusion:

Utilizing existing experience working with Varileog and picking up new abilities, including utilizing an oscilloscope, I was able to successfully finish this lab. This lab taught me how to use the oscilloscope to evaluate design modules such as the counter in Verilog using the FPGA board. I also learnt how to develop a debounce circuit to get rid of electrical chatter in a design, as well as how to use the package pin numbers on the ZYBO board to create an XDC file for the top-level design module. The significance of a debounce circuit and how it works were also important lessons I learned from this lab.

Post-Lab Deliverables

1. ***Include the source code with comments for all modules in lab. You do not have to include test bench code. Code without comments will not be accepted!***

This is all included above in the **Design** section.

2. ***Include any XDC files that you wrote or modified.***

This is all included above in the **Design** section.

3. ***Include screenshots of all waveforms captured during simulation in addition to the test bench console output for each test bench simulation.***



Figure 9: Waveform for Up-Counter



Figure 10: Waveform for Up-Counter with Hexadecimal Output

```
# }
# run 1000ns
INFO: [USF-XSim-96] XSim completed. Design snapshot 'up_counter_tb_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
```

Figure 11: Console Output for Up-Counter and Up-Counter with Hexadecimal Output

 


Figure 12: Waveform for No Debounce

```
# }
# }
# run 3000ns
INFO: [USF-XSim-96] XSim completed. Design snapshot 'bounce_tb_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 3000ns
```

Figure 13: Console Output for No Debounce

 


Figure 14: Waveform for With Debounce

```
# }  
# }  
# run 3000ns  
INFO: [USF-XSim-96] XSim completed. Design snapshot 'bounce_tb_behav' loaded.  
INFO: [USF-XSim-97] XSim simulation ran for 3000ns
```

Figure 15: Console Output for With Debounce

4. Answer all questions throughout the lab manual.

- a. Experiment Part 1, 4.a (clock periods and answer the question): How do your count signals differ from the original clock signal?**

COUNT2 = 128.00ns
COUNT3 = 64.00ns
COUNT4 = 512.00ns
COUNT5 = 256.00ns

These are as expected - the counters are uniformly dividing the clock signal in multiples of 2.

- b. Experiment Part 2, 2.b: You should see that the test bench produces a Clk signal. What is the frequency of that signal?**

$F = 1/T_c$; so Freq = $1/10\text{ns} = 10000 \text{ MHz} = 10 \text{ BHz}$

- c. Experiment Part 2, 2.c: You should also see that the test bench holds the counter in reset for a specific interval of time. How long is that interval?**

Reset interval = 20 ns.

- d. Experiment Part 2, 2.d: After reset is de-asserted, the test bench holds the enable LOW for some amount of time before allowing the counter to run. How long is this time period?**

Time period is 20ns.

- e. Experiment Part 2, 2.f: Finally, you should notice that the counter will roll over after reaching a maximum value. What is this maximum count value and what signal in the waveform could we use to know exactly when the counter is going to roll over?**

Maximum count is 1111 (F in hexadecimal); the counter will roll over when Carry3 is equal to 1.

- f. Experiment Part 2, 3.a: If we use a 125MHz clock to drive our frequency divider, what rate will the most significant bit of the divider oscillate at?**

Frequency = $(125\text{MHz}) / 2^{26} = 1.86 \text{ Hz}$

Time = $1/f = 1/1.86\text{Hz} = 0.537 \text{ s}$

- g. Experiment Part 3, 1.b: Does the circuit in 'noDebounce.v' work as expected? Why or why not?**

Yes, the circuit in the module is working as expected. You can see the electrical noise (no debouncing is used) in Figure 12, which is the blank outputs between the valid number outputs. For example, at the output is 0000 there's a space with no output (".") and then it turns into 0001. Without a debounce circuit, we can see the switch bounce within the waveform and this can be fixed by implementing debounce in the design.

- h. Experiment Part 3, 2.a: Does the counter in 'withDebounce.v' work as expected? Why or why not?**

The "withDebounce.v" module also works as expected which is shown clearly in Figure 14. While there is still electrical noise, it does not affect the output like it did in Figure 12. For example, when the output switches from 0000 to 0001 there is no noise between the two outputs. So the debounce is working well and correctly as intended.

- i. Experiment Part 3, 2.c: Explain in your lab write-up the operation of the circuit described in 'withDebounce.v'. Use waveforms to compare operation of noDebounce and withDebounce.**

Figure 7 shows the Verilog code for withDebounce.v with comments explaining each line of code. We can see that there are two flip-flop synchronizers operating on the positive edge of the clock. There are also enable and reset inputs that operate on the positive edge of the clock and take 1 and 0 as inputs, respectively. You can also see the AND and NOT gates connected from the output of the synchronizer to the enable and reset inputs of the binary counter. The output of the binary counter (Msb) passes

through the NOT gate and into the AND gate with the synchronizer output. The final output of the debounce circuit is Msb.

Looking at the differences between the waveforms in Figure 12 and Figure 14 (noDebounce vs withDebounce), there is also a clear change in behavior between the two circuits. With noDebounce, we see the signal bounces after the user input, however, with withDebounce, we do not see any signal bounce because of the debounce circuit being implemented.

Important Student Feedback

1. What did you like most about the lab assignment and why? What did you like least about it and why?

What I liked most about this lab assignment was that I was able to keep practicing with Verilog, as I appreciate gaining more much needed experience. I also had fun using the oscilloscope. What I most liked was just the general tedium of having to troubleshoot my code.

2. Were there any sections of the lab manual that were unclear? If so, what was unclear? Do you have any suggestions for improving the clarity?

The lab manual was clear and concise to understand.

3. What suggestions do you have to improve the overall lab assignment?

I do not have any suggestions to improve the lab assignment.